



Quiz (9)

18th December 2012

Time duration: 10 minutes

Prepared by: Dr. Hessa Al-Junaid

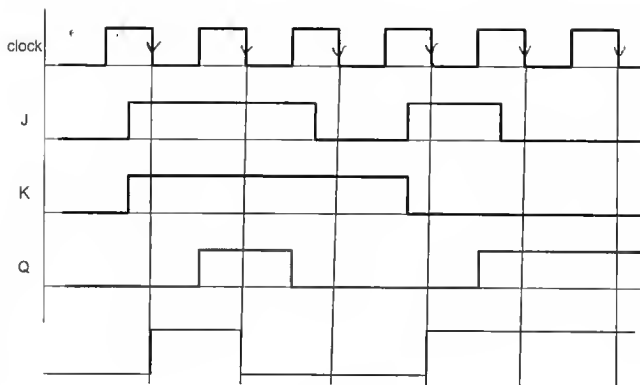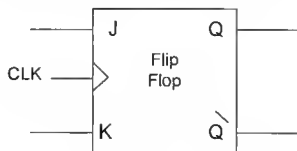Complete the following timing diagram for a J-K Flip Flop shown in the figure.



rising
edge
falling
edge: